

## 1.8 TABULATION

## Transient Analysis

	Amplitude	Frequency	Phase difference
Input signal	50 mV	1kHz	
Output signal	10V	1kHz	180°

(a)

## Frequency Response

$$Vi = 50\text{mV}$$

Frequency (Hz)	Output Voltage (Vo) (V)	Gain (Av)	Gain in db $Av = 20 \log(Vo/Vi)$
20	5	5	13.9
30	6	6	15.5
40	7	7	16.9
50	9	9	19.0
100	10	10	20.0
200	11	11	20.8
300	12	12	20.8
900	12	12	21.5
1k	12	12	21.5
2k	12	12	21.5
3k	12	12	21.5
4k	12	12	21.5
5k	12	12	21.5
6k	12	12	21.5
50k	12	12	21.5
100k	12	12	21.5
200k	11	11	20.8
300k	10	10	20.0
400k	9	9	19.0
500k	8	8	18.0

(b)

of CE amplifier.


E amplifier.


### 1.10 POSTLAB QUESTIONS

1. How do coupling capacitors  $C_1$  and  $C_2$  affect the frequency response? Why?
2. What is the effect on the amplifier performance of omitting  $R_E$ ?
3. What is the effect on input impedance of removing bypass capacitor  $C_E$ ?
4. (a) What is the phase relationship between the input and output signals of a CE amplifier?  
(b) Was this relationship confirmed by the results of your experiments? Explain how.
5. Is the output impedance of a Common emitter amplifier a fixed quantity? Confirm your answer by referring specifically to any substantiating data in this experiment.
6. From a measurement of the rise time of the output pulse of an amplifier, whose input is a small amplitude square wave, one can estimate the \_\_\_\_\_ parameter of the amplifier.
7. What is the effect found when  $V_{CE} > V_{CC}/2$ ?

### 1.11 RESULT

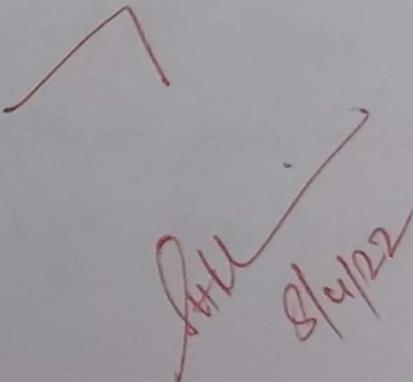- a. The phase difference between the input and output voltage waveform is  $180^\circ$
- b. The Mid-band voltage gain =  $18.5 \text{ dB}$
- c. The Lower cutoff frequency =  $50 \text{ Hz}$
- d. The Upper cutoff frequency =  $300 \text{ KHz}$
- e. Bandwidth =  $300 \text{ K} - 50 \text{ Hz}$   
 $= 299.95 \text{ KHz}$



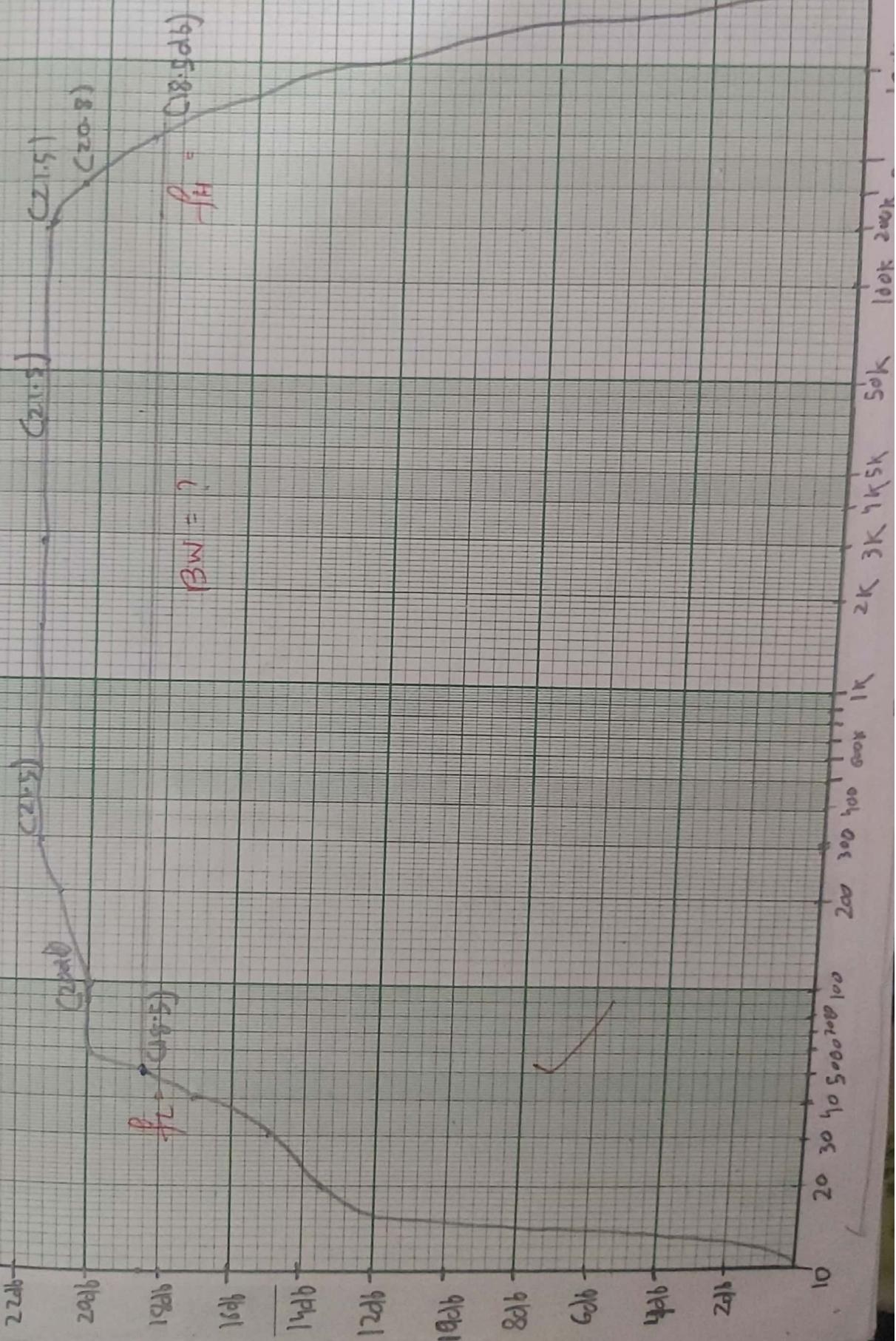

## INPUT WAVEFORM



Scale

X-axis  $\rightarrow$  1 unit = 0.25 ms

Y-axis  $\rightarrow$  1 unit = 2.5 mV

## Output waveform



Scale

X-axis  $\rightarrow$  1 unit = 0.25 ms

Y-axis  $\rightarrow$  1 unit = 1 mV



## 2.7 TABULATION

## CS MOSFET AMPLIFIER WITH CURRENT-SERIES FEEDBACK :-

## Transient Analysis

(environ)

(Ic)

(C00)

	Amplitude	Frequency	Phase difference
Input signal	5 mV	1 kHz	
Output signal	200 mV	1 kHz	180°

(a)

## Frequency Response

Frequency	Output Voltage (Vo)	Gain	Vi = 100mV Av = 20 log(Vo/Vi) Gain in db
20 Hz	18 V	18	25 db
30 Hz	26 V	26	28 db
40 Hz	30 V	30	29.5 db
50 Hz	32 V	32	29.6 db
60 Hz	33.6 V	33.6	30 db
100 Hz	33.5 V	33.5	30 db
1 kHz	37 V	37	31 db
2 kHz	37 V	37	31 db
3 kHz	37 V	37	31 db
4 kHz	37 V	37	31 db
10 kHz	37 V	37	31 db
20 kHz	36 V	36	31 db
30 kHz	35 V	35	31 db
40 kHz	34 V	34	30 db

Expt-2

20

50 KHz	33V	33	30db
100 KHz	26V	26	28db

(b)

### S MOSFET AMPLIFIER WITH VOLTAGE-SERIES FEEDBACK :-

#### Transient Analysis

	Amplitude	Frequency	Phase difference
Input signal	5 mV	1KHz	180°
Output signal	100 mV	1K Hz	

(c)

$V_i = 100mV$

#### Frequency Response

Frequency	Output Voltage $V_o$	Gain	Gain in db $A_v = 20 \log(V_o/V_i)$
20 Hz	2.46 V	2.46	8
30 Hz	4.62	4.62	13
40 Hz	6.59	6.59	16
50 Hz	8.17	8.17	18.35
100 Hz	13.08	13.08	22.39
200 Hz	15.79	15.79	24
300 Hz	16.47	16.47	24.35
400 Hz	16.97	16.97	24.35
500 Hz	16.47	16.47	24.35
1 KHz	16.47	16.47	24.35
2 KHz	16.47	16.47	24.35
3 KHz	16.47	16.47	24.35
10 KHz	16.47	16.47	24.35
20 KHz	16.47	16.47	24.35
100 KHz	15.30	15.30	23.7
200 KHz	12.17	12.17	21.66
300 KHz	9.60	9.60	19.629
500 KHz	6.44	6.44	16.27
1 MHz	3.50	3.50	


#### 2.10 RESULT:



1. The current series and voltage series feedback amplifier were designed and its frequency response was plotted.
2. The following parameters were observed.




CS MOSFET Amplifier

CS MOSFET Amplifier		Mid Band Voltage Gain	Bandwidth
Current Series Amplifier	With Feedback	28 dB	$100 \frac{K_{n2}}{2} - 20 Hz$ $\approx 99.17 K_{n2}$
	Without Feedback		
Voltage Series Amplifier	With Feedback	31.35 dB	$200 \frac{K_{n2}}{2} - 90 Hz$ $\approx 119.17 K_{n2}$
	Without Feedback		

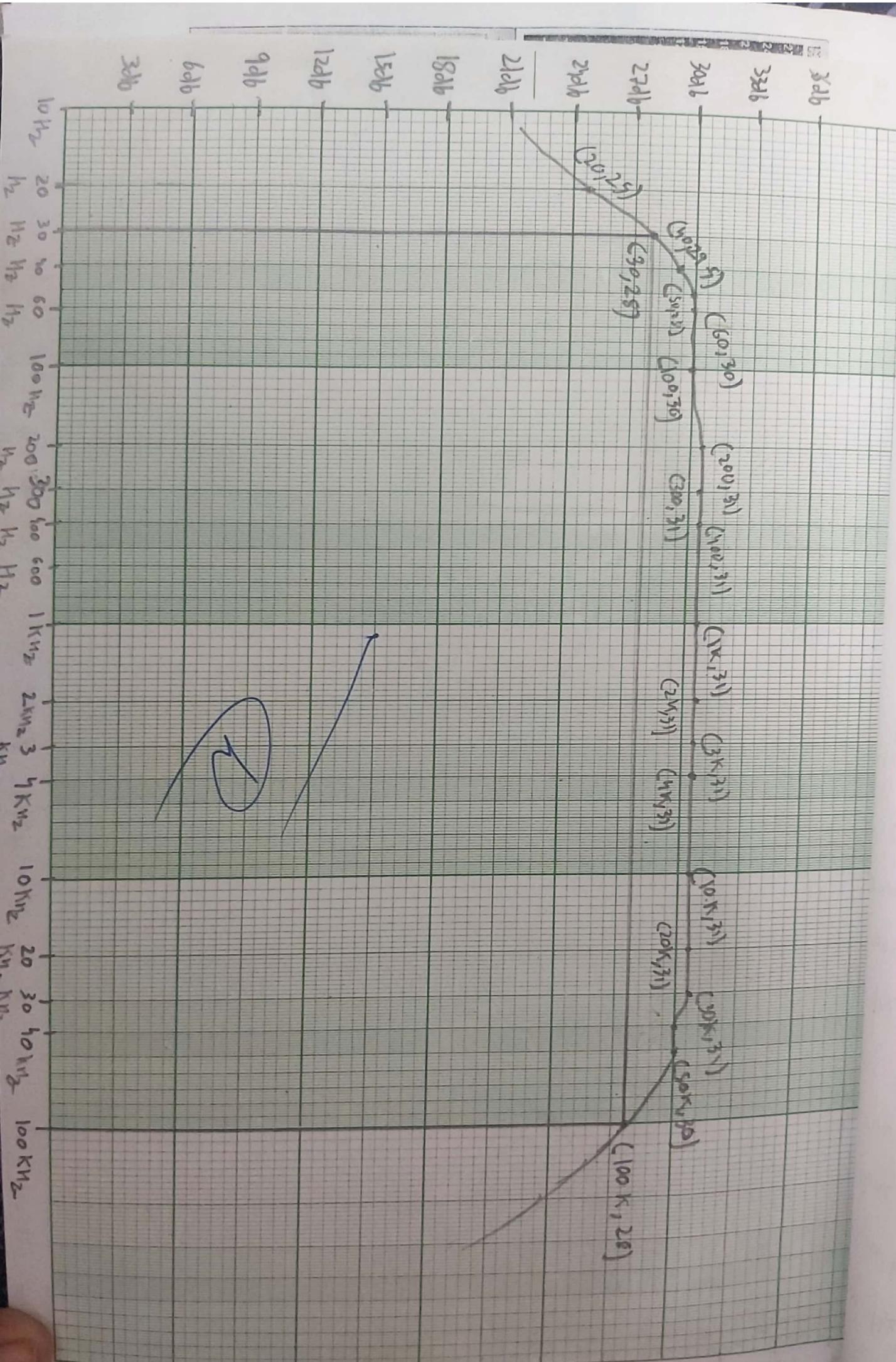

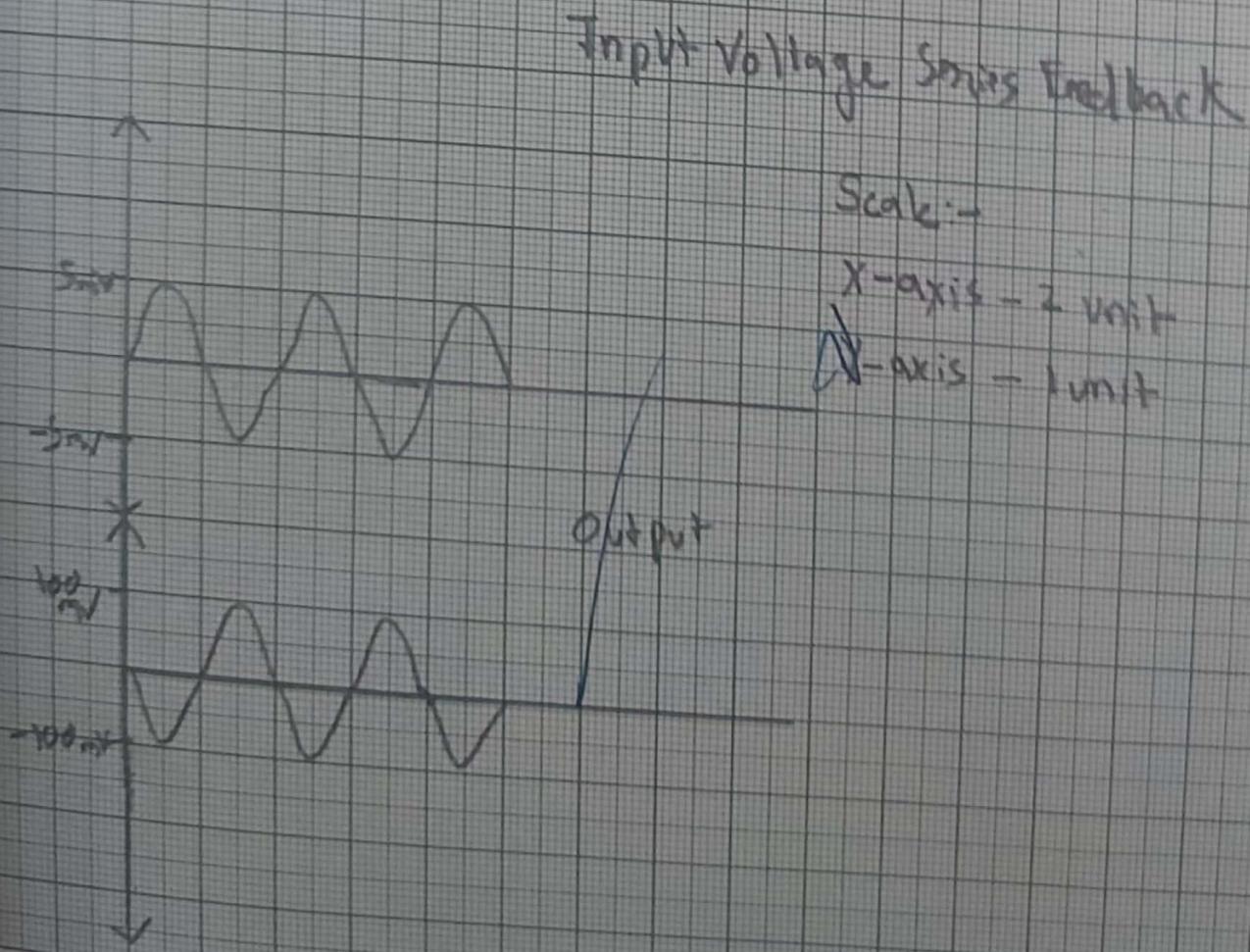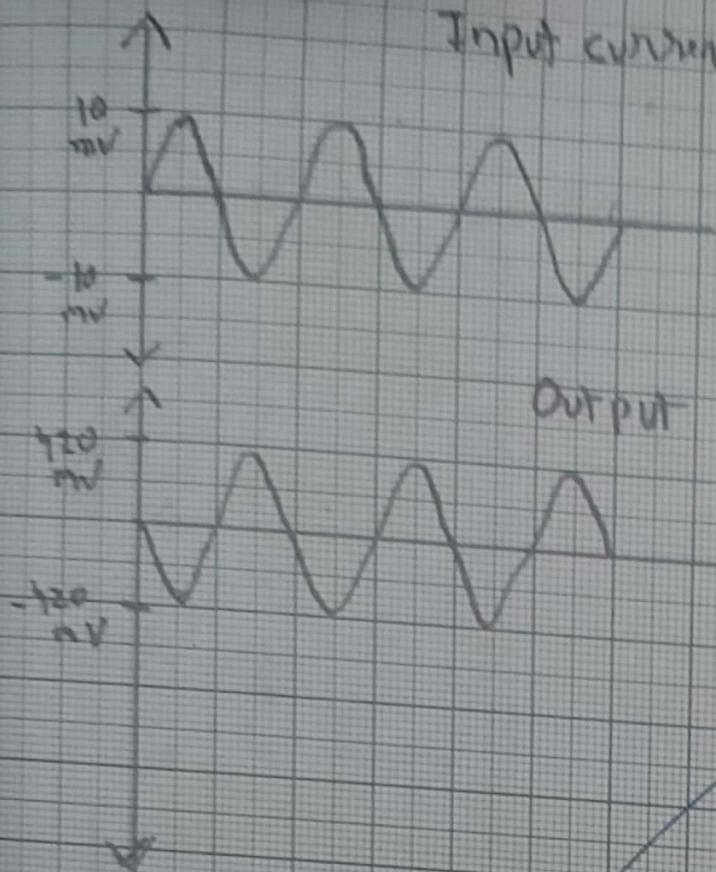

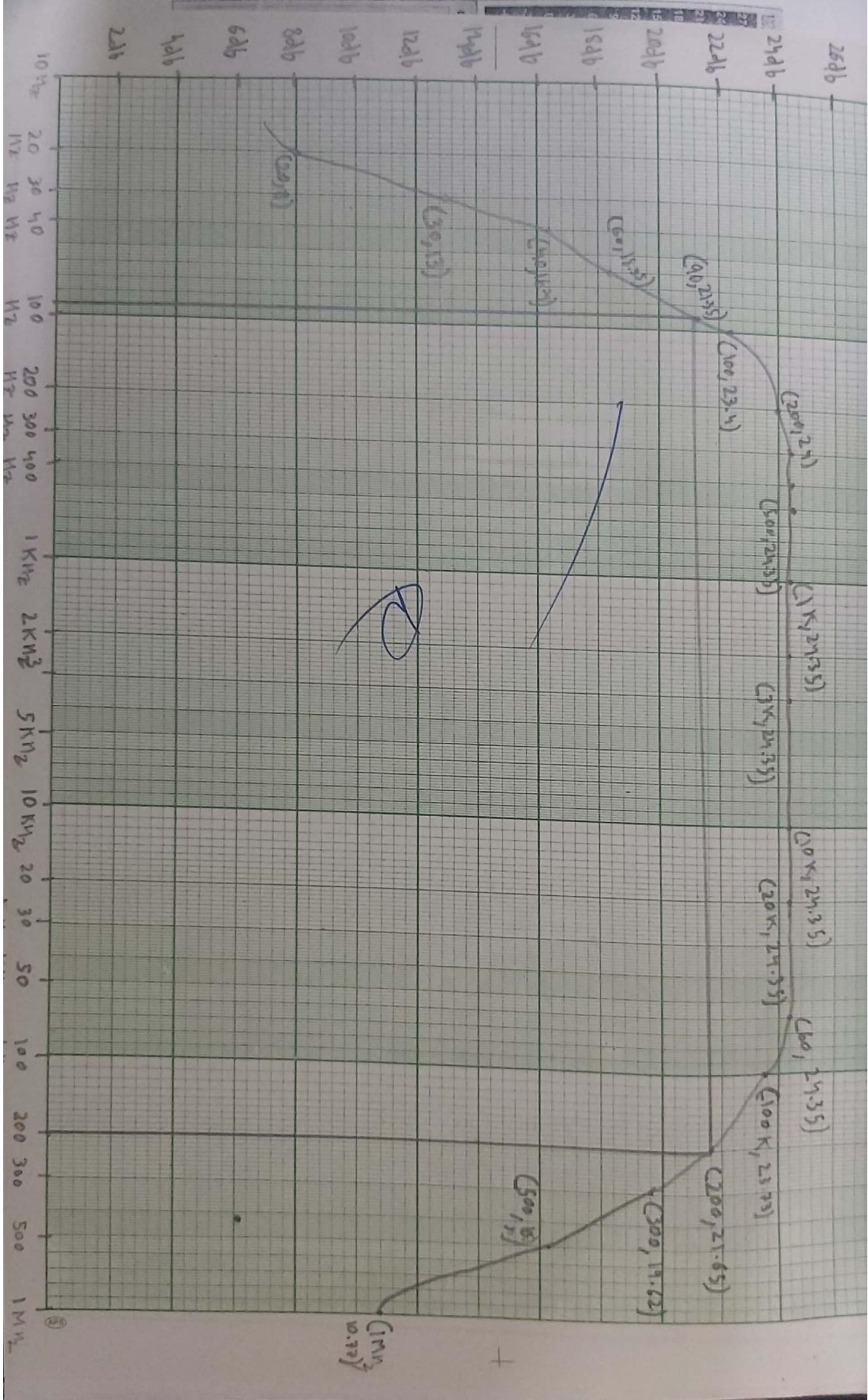

frequency across  $R_L$ . Take atleast 10 readings and tabulate the reading in Table. Plot on

a semi log graph sheet the frequency response (voltage gain Vs frequency) curve using the above measurements.

- d. From the plot, determine the values of (a) Mid band voltage gain,  $A_v(\text{mid})$ , (b) Lower cut-off frequency, (c) upper cut-off frequency and (d) Bandwidth.

### 3.8 TABULATION

#### Transient Analysis

	Amplitude	Frequency	Phase difference
Input signal	100 mV	1K	0
Output signal after 1 <sup>st</sup> transistor	0.1 V	1K	180
Output signal after 1 <sup>st</sup> transistor	13 V	1K	180

#### Frequency Response

$$V_i = 1\sqrt{V} \text{ V}$$

Frequency	Output Voltage $\sqrt{V}$ (Vo)	Gain	Gain in db $A_v = 20 \log(Vo/Vi)$
10 Hz	4	4	12
20 Hz	8.5	8.5	18
30 Hz	12	12	21.2
40 Hz	14.5	14.5	23.5
100 Hz	24	24	28
200 Hz	28.1 V	28.1	29
300 Hz	29 V	29	29.2
1 KHz	29.8 V	29.8	29.2
2 KHz	29.8 V	29.8	29.2
3 KHz	29.8 V	29.8	29.2

1 MHz	29.8 V	29.8	29.5
2 MHz	29 V	29	29.2
3 MHz	28.1 V	28.1	29
10 MHz	19.5 V	19.5	25.9
20 MHz	12 V	12	21.5

1 MHz	29.8 V	29.8	29.5
2 MHz	29 V	29	29.2
3 MHz	28.1 V	28.1	29
10 MHz	19.5 V	19.5	25.9
20 MHz	12 V	12	21.5

## 9 PRELAB QUESTIONS

In what ways the Cascode amplifier has advantage over CE amplifier?

Why the analysis of Transistor circuit is split in to AC while keeping all the DC source equal to zero and DC while keeping all the AC source equal to zero.

What does the term small signal imply?

Discuss the construction of Cascode amplifier.

What are the physical meaning of hybrid  $\pi$  parameters  $r_\pi$ ,  $r_o$ .

## 10 POSTLAB QUESTIONS


Compare the AC characteristics of CE amplifier and cascade amplifier.

Discuss the general conditions under which the cascade amplifier would be used.


Compare the transient characteristics of input signal and output signal.
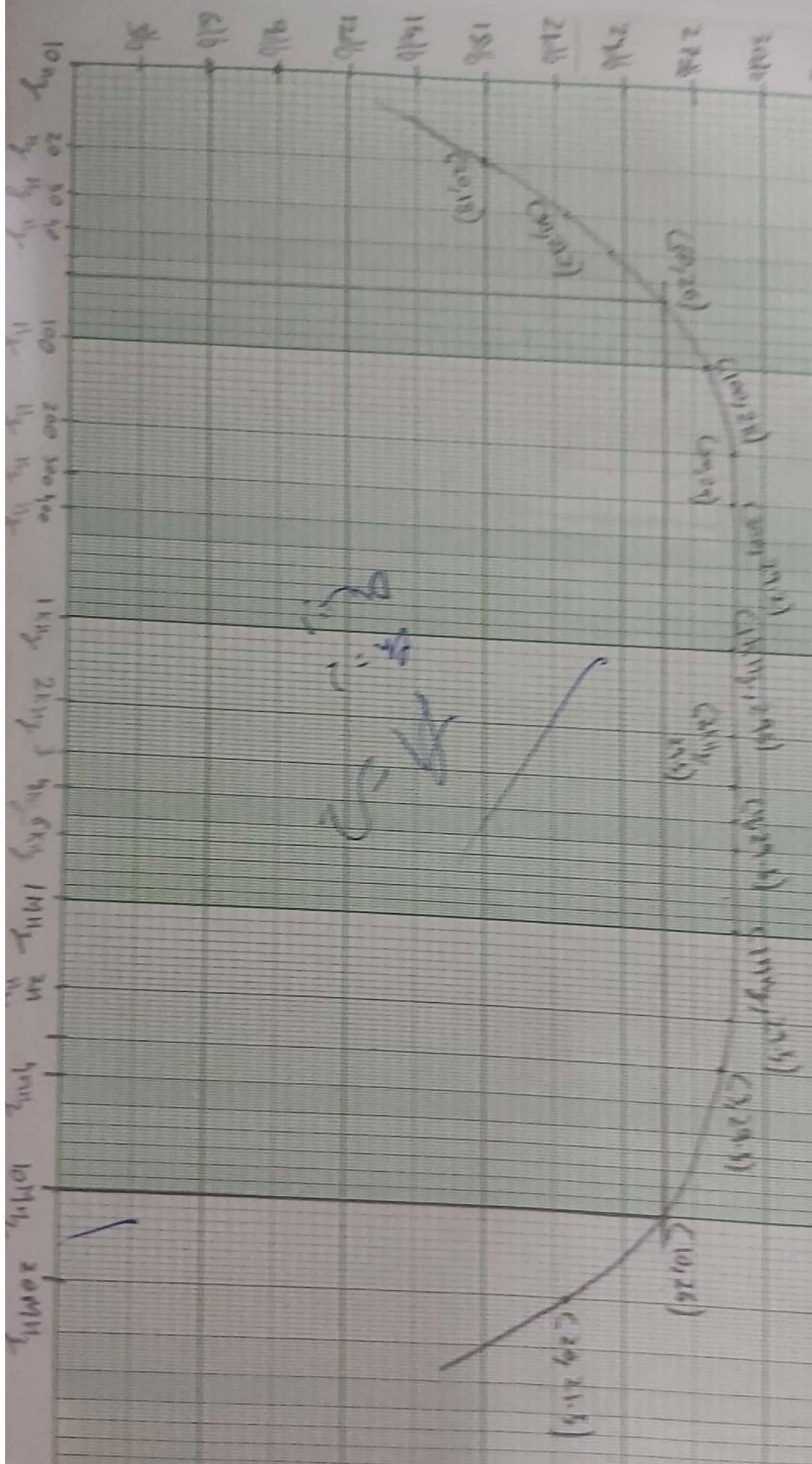
## 11 RESULT


- The phase difference between the input and output voltage waveform is  $180^\circ$
- The Mid-band voltage gain = 26.2 db
- The Lower cutoff frequency = 50 Hz
- The Upper cutoff frequency = 9 kHz
- Bandwidth=  $9\text{kHz} - 50\text{Hz} \approx 9\text{kHz}$



Input Waveform

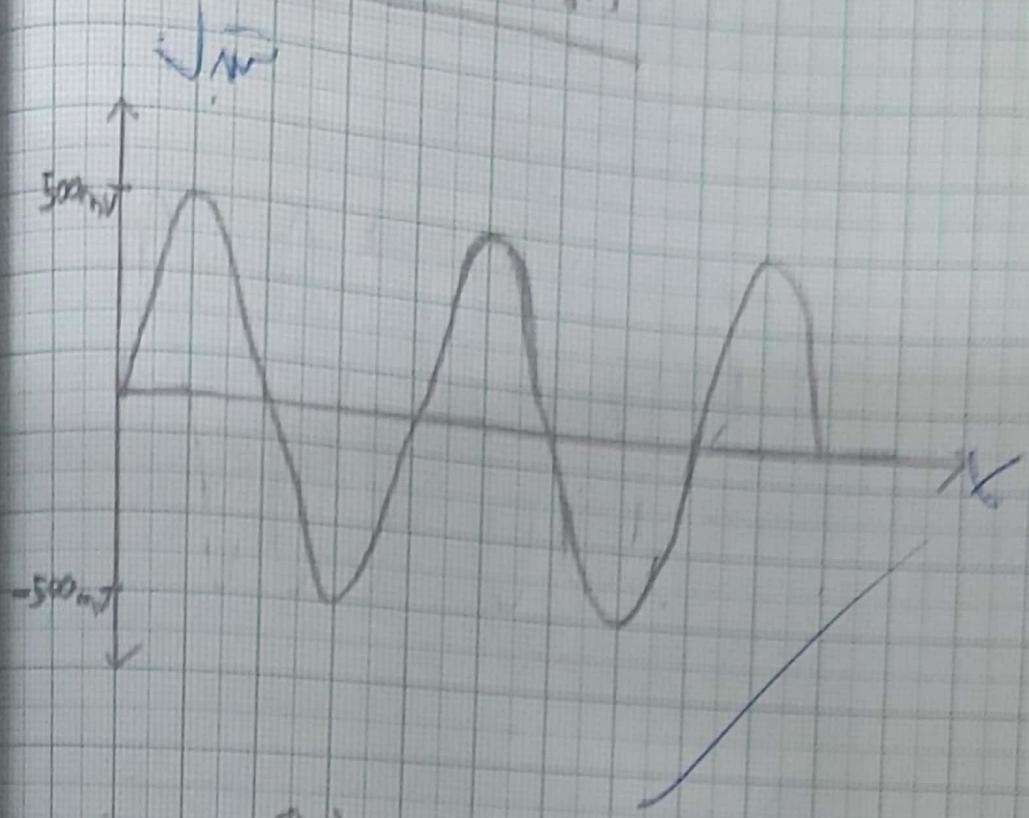

Output Waveform

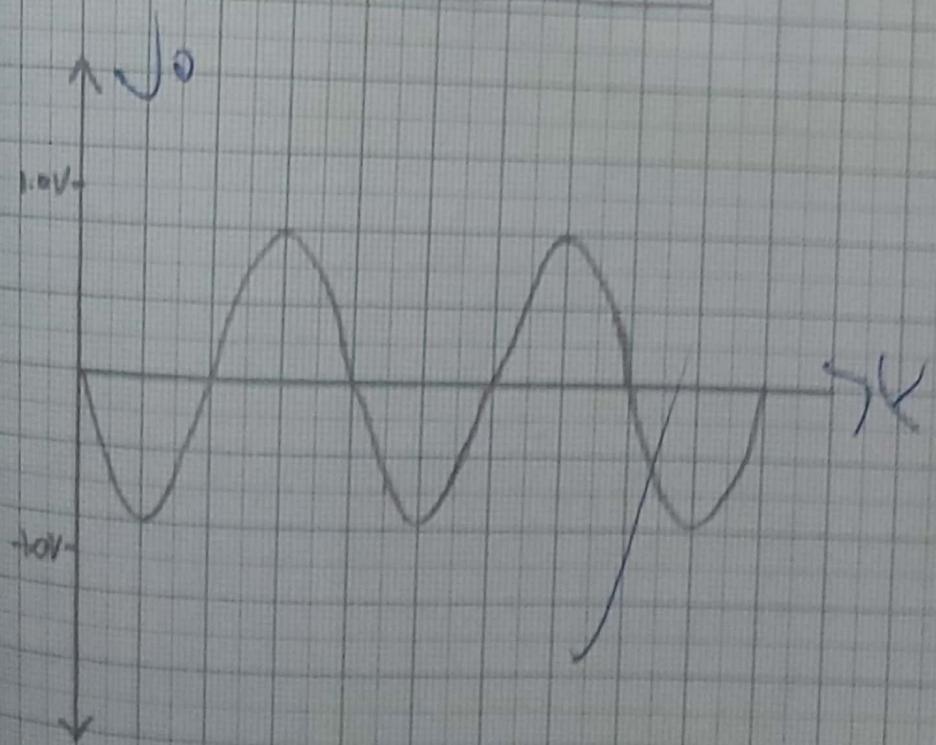

$$1.5\text{KHz} = \frac{1}{2\pi R * 0.1\mu F * \sqrt{6}}$$

$$R = 3.3 \text{ K}\Omega$$

#### 4.5.1 Design Constraints

1. Frequency of oscillation is proportional to  $f = \frac{1}{2\pi RC\sqrt{2N}}$ , where N is the number of stages.

Thus RC phase shift oscillator at higher frequencies have high phase noise which results in instability in frequency as number of stages increases.

2. It requires very small resistor value which is difficult to realize on chip.

#### 4.6 PROCEDURE

1. Connections are made as shown in the circuit diagram.
2. The DC power supply is switched ON.
3. The output waveform is displayed on the CRO.
4. The peak to peak Amplitude and time period of the sine wave is noted.
5. The graph of output waveform is drawn.

#### 4.7 TABULATION

	Amplitude (Volts)	Time period(sec)	Frequency (Hz)
Practical value	$3.8 \times 2 = 7.6V$	1 ms	1 KHz
Theoretical value	7.6V	0.5 ms	1.5 KHz

✓ 0.10  
Value  
ms

#### 4.8 PRE LAB QUESTIONS

1. What is Phase shift oscillator?
2. What is the difference between RC phase shift oscillator and LC oscillator?
3. What is the condition for sustained oscillation in RC phase shift oscillator?
4. What is the equation for RC phase shift oscillator?
5. What are the applications of RC phase shift oscillators?


#### 4.9 POST LAB QUESTIONS


1. Why we need a phase shift between input and output signal?
2. Why RC oscillators cannot generate high frequency oscillations?

3. What difference will the number of sections(R&C) in the oscillator circuit make?
4. How is phase angle determined in RC phase shift oscillator?
5. How can we get a maximum phase angle of 90° in RC phase shift oscillator?
6. What is the maximum frequency for which a RC phase shift oscillator can be designed without any distortion in phase?

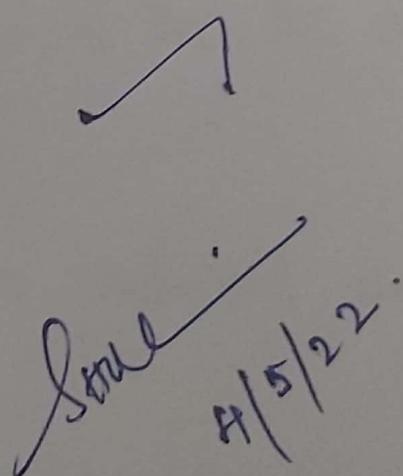
#### 4.10 RESULT

Thus an RC phase shift oscillator is designed, constructed and tested. Frequency of oscillation Theoretical  $f_T = \text{[circled 220]} \text{ Hz}$ , Practical  $f_p = 7.6 \text{ V}$



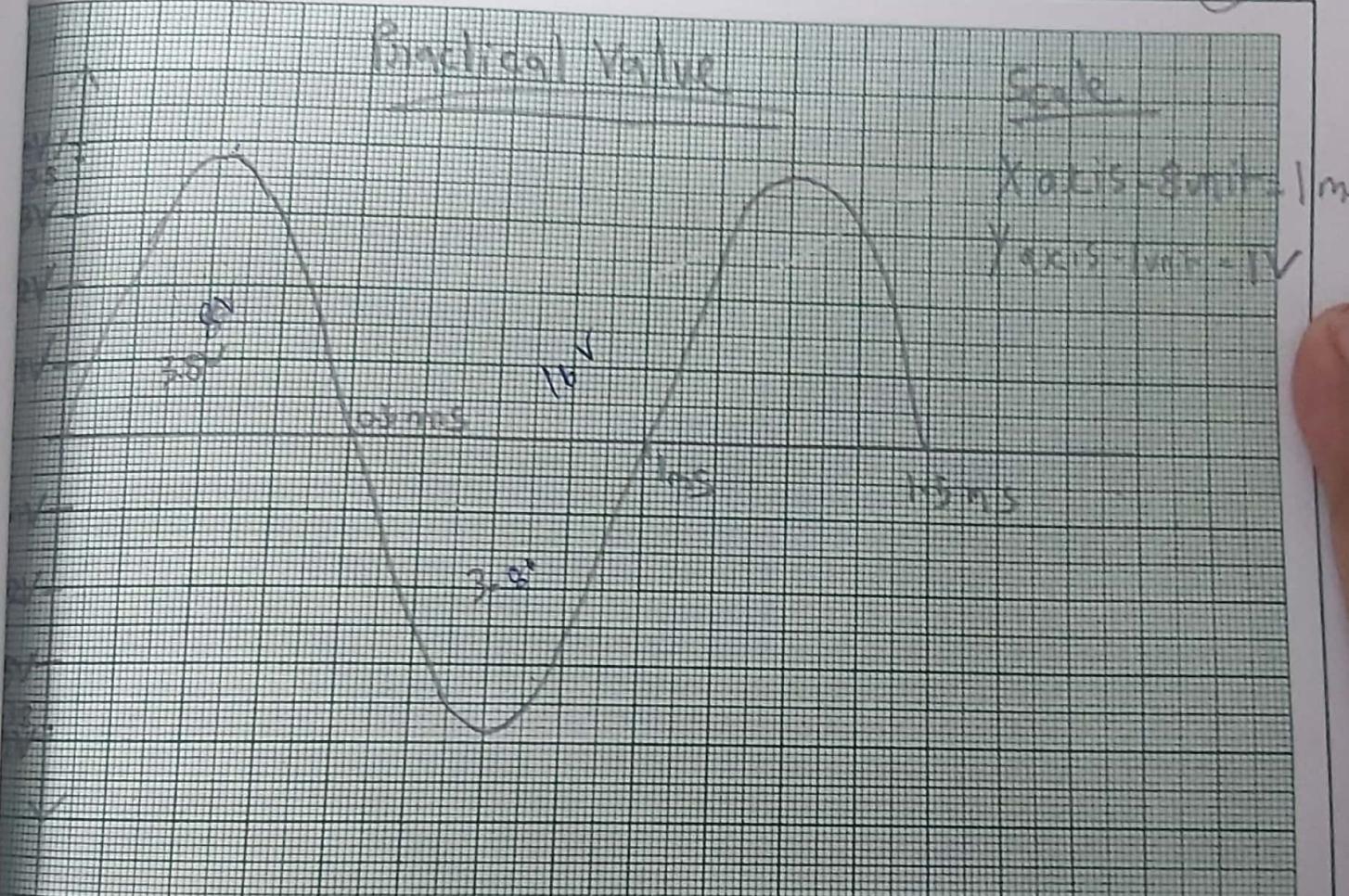

Theoretical Value

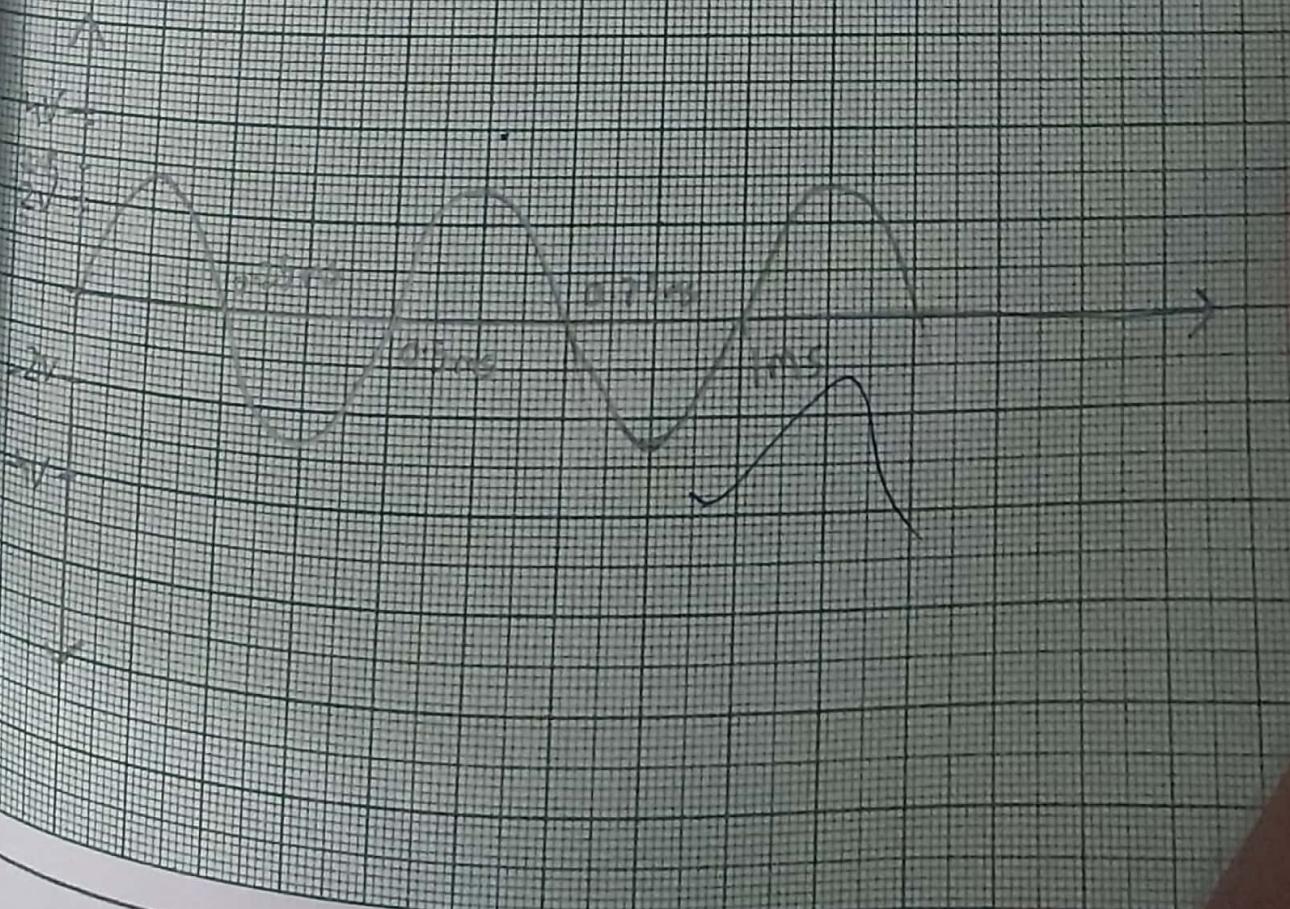

6. Calculate the common mode rejection ratio  $CMRR = A_d/A_c$ .

## 66 TABULATION

## Input and Output Voltage Signal Measurements

Mode	Input Voltage	Output Voltage	Frequency	Voltage Gain	Phase Difference
Differential Mode	$V_{in1} = 50mV$ $V_{in2} = 0V$	$V_{o1} = 1.6 \times 2 = 3.2$ $V_{o2} = 1.4 \times 2 = 2.8$ $V_o = V_{o1} - V_{o2}$ = 0.4	1KHz	120	$180^\circ$
Common Mode	$V_{in1} = 50mV$ $V_{in2} = 50mV$	$V_{o1} = 2.80mV$ $V_{o2} = 2.80mV$ $V_o = V_{o1} - V_{o2}$ = 0	1KHz	0	$0^\circ$

$$CMRR = \frac{\text{Differential Mode Gain}}{\text{Common Mode Gain}} =$$

## Frequency Response

Frequency	Output Voltage ( $V_o$ )	Gain	$V_i = 50mV$ $A_v = 20 \log(V_o/V_i)$
30	$V_{o1} = -1.8$ $V_{o2} = 1.6$	64	36.12
69	$V_{o1} = 2.6$ $V_{o2} = 2.2$	96	39.64
180	$V_{o1} = -3.2$ $V_{o2} = 2.8$	120	41.58
24.9 KHz	$V_{o1} = -2.0$ $V_{o2} = 2.2$	96	89.69

130 KHz       $V_{o1} = -2$   
 $V_{o2} = 1.6$  }  $V_o = -3.6$       72      33.17

4. A change

in emitter resistance  $R_E$  in a differential amplifier

- (a) affects the difference mode gain  $A_d$
- (b) affects the common mode gain  $A_c$
- (c) affects both  $A_d$  and  $A_c$
- (d) does not affect either  $A_d$  and  $A_c$

5. Find the CMRR if differential voltage gain and common mode voltage gain of a differential amplifier are 48db and 2 db respectively.

## 6.9 RESULT

Thus the differential amplifier was constructed and dc collector current for the individual transistor is determined. The CMRR is calculated as

$$\text{CMRR} = \frac{\infty}{0}$$

$\text{CMRR} = 160^2$

3. Connect an oscilloscope to the output of the circuit. Adjust the output of the sine-wave generator until undistorted. Maximum signal output is obtained.

4. Observe and measure the peak-to-peak amplitude of input and output signal and record the values in the tabulation provided.

5. Now, sweep the input signal frequency in the range 30Hz to 1 MHz by adjusting the sine wave generator output.

6. For each setting of input frequency, measure the output signal voltage.

7. Draw the frequency response curve on a semi-log graph sheet. From this plot, obtain the values of mid-band voltage gain, upper and lower cut-off frequency and BW (f<sub>l</sub>).

### Frequency Response of Amplifier without Negative Feedback

1. Remove R<sub>f</sub> from the circuit and connect RE and CE directly to the emitter terminal.

2. Measure and record in the table, the frequency response of this circuit without R<sub>f</sub> by repeating steps 5 through 6.

### 7.7 TABULATION

Measurement of frequency response of current series feedback amplifier

$$V_{in} = 50mV$$

Frequency (in Hz)	V <sub>o</sub> (Volts)	Gain = V <sub>o</sub> /V <sub>in</sub>	Gain (dB) = 20 log(V <sub>o</sub> /V <sub>in</sub> )
10	0.23	4.6	13.2
20	0.32	6.4	16.12
80	0.34	6.8	16.65
100	0.35	7	16.90
1 K	0.35	7	16.90
30K	0.35	7	16.90
100K	0.35	7	16.90
350K	0.35	6.4	16.90
470K	0.32	5.6	16.12

500	0.28	5.6	14.96
760	0.24	4.8	13.62
900	0.22	4.4	12.86

58

Measurement of frequency response of amplifier without feedback

$$V_{in} = 50 \text{ mV}$$

Frequency (in Hz)	$V_o$ (Volts)	$\text{Gain} = V_o/V_{in}$	$\text{Gain (dB)} = 20 \log(V_o/V_{in})$
50	3.6	72	37.146
110	4.8	96	39.64
250	5.2	104	40.34
800	5.6	112	40.98
10K	5.6	112	40.98
14K	5.6	112	40.98
19K	5.6	112	40.98
22K	5.4	108	40.34
60K	5.2	104	39.64
200K	4.4	88	38.04
600K	2.4	48	32.04
900K	2	40	30.10
1600K	1.2	24	27.60

#### 7.8 PRELAB QUESTIONS:

- What do you understand by feedback in amplifiers?

3. What is the formula for input resistance of a current series feedback amplifiers?
4. What is the effect of negative feedback on the bandwidth of an amplifiers?
5. What are the fundamentals assumptions that are made in feedback amplifiers?

### 7.10 RESULT:

4. The current series feedback amplifier was designed, constructed and its frequency response was plotted.
5. The following parameters were observed.

Frequency response data	Current series feedback Amplifier	Current series Amplifier without feedback
Mid_band Voltage Gain	40.98 dB	16.10
Bandwidth	10K-110Hz	400K-12Hz

2. The DC power supply is switched ON.
3. The output waveform is displayed on the CRO.
4. The peak to peak Amplitude and time period of the sine wave is noted.
5. The graph of output waveform is drawn.

### 8.8 TABULATION

	Amplitude (Volts)	Time period(sec)	Frequency (Hz)
Practical value	2V	12ms	83.33K Hz
Theoretical value	2V	10ms	100.1 KHz

all  
values  
are  
approximate.

## Practical


Scale:

X axis:

$$2 \text{ units} = 6 \mu\text{s}$$

Y axis:

$$2 \text{ units} = 1 \text{ V}$$

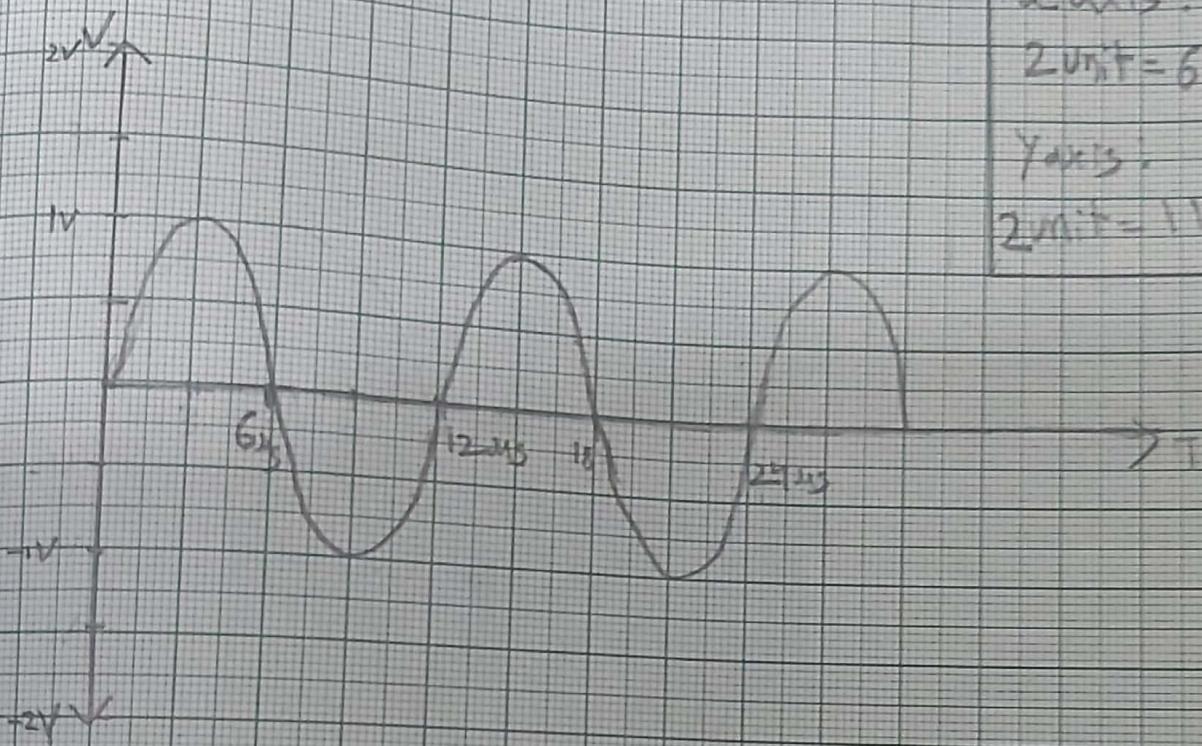


## Theoretical

Scale:

$$2 \text{ units} = 2 \mu\text{s} = 5 \mu\text{s}$$
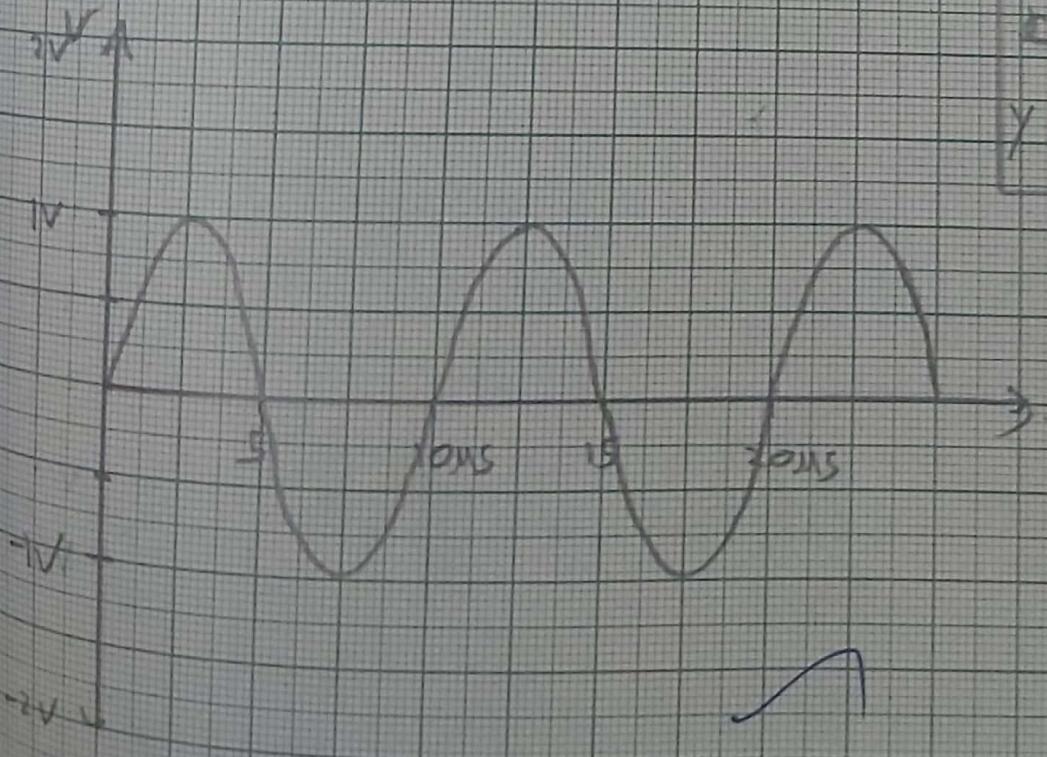
$$Y \text{ axis: } 2 \text{ units} = 1 \text{ V}$$



I<sub>1</sub>

1.9 mA

2.8 mA

3.7 mA

4.6 mA

5.5 mA

I<sub>G1</sub>

1.91 mA

2.8 mA

3.7 mA

4.6 mA

5.5 mA

Exp 9

OP Vertical.  
M  
HKB<sub>2</sub>

<u><math>I_1</math></u>	<u><math>I_{C_1}</math></u>
1.9 mA	1.92 mA
2.8 mA	2.85 mA
3.4 mA	3.1 mA
4.5 mA	4.55 mA
5 mA	5.1 mA

Fxp-10

C  
ob105k

Verh

## Wilson Current Mirror

11

$I_C$

1.2 mA  
1.6 mA  
1.8 mA  
2.2 mA  
2.6 mA  
3.6 mA  
7.5 mA

$I_{C2}$

1.24 mA  
1.61 mA  
1.81 mA  
2.23 mA  
2.63 mA  
3.7 mA  
7.6 mA

## Cascode Current Mirror

$I_{C1}$

1.2 mA  
1.6 mA  
1.8 mA  
2.2 mA  
2.6 mA

$I_{C2}$

1.24 mA  
1.61 mA  
1.81 mA  
2.23 mA  
2.63 mA

Fig 12.5 Output frequency response plot

## 12.6 TABULATION

$$V_i = \underline{1000 \text{ mV}} = 1 \text{ V}$$

S.No	Freq	$V_o$ (volts)	$\text{Gain} = V_o/V_i$	Gain in dB
1Hz		11.05	11.05	20.6
2Hz		17.79	17.79	25.18
3Hz		22.25	22.25	27.02
6Hz		27.49	27.49	28.78
30Hz		30.22	30.22	29.6
50Hz		30.22	30.22	29.6
70Hz		30.22	30.22	29.6
10KHz		30.22	30.22	29.6
12.1KHz		29.9	29.9	29.52
40KHz		26.9	26.9	28.59
70KHz		22.0	22.0	27.97
160KHz		18.59	18.59	25.34